

# 數位邏輯實習


栓鎖器、正反器

國立台北科技大學  
電機工程系  
吳昭正


# Outline

- 栓鎖器(Latch)
- 正反器(Flip-Flop)
- Digital的正反器與時脈產生器
- VHDL語法介紹
- 作業題

# S-R Latch(1/2)

 


(a)

 


(b)

# S-R Latch(2/2)

 


S R	$Q^+$
0 0	Q
0 1	0
1 0	1
1 1	Not allowed

# D Latch(1/2)

 


(a)

 


(b)

# D Latch(2/2)

 


$G$	$D$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# D Flip-Flop(1/2)

 

(a) Rising-edge trigger

 


(b) Falling-edge trigger

$D$	$Q$	$Q^+$
0	0	0
0	1	0
1	0	1
1	1	1


(c) Truth table

$$Q^+ = D$$

# D Flip-Flop(2/2)

 

 
(a) Construction from two gated D latches



(b) Time analysis



# S-R Flip-Flop(1/2)

 

Operation summary:


$S = R = 0$  no state change

$S = 1, R = 0$  set Q to 1 (after active Ck edge)


$S = 0, R = 1$  reset Q to 0 (after active Ck edge)

$S = R = 1$  not allowed

# S-R Flip-Flop(2/2)

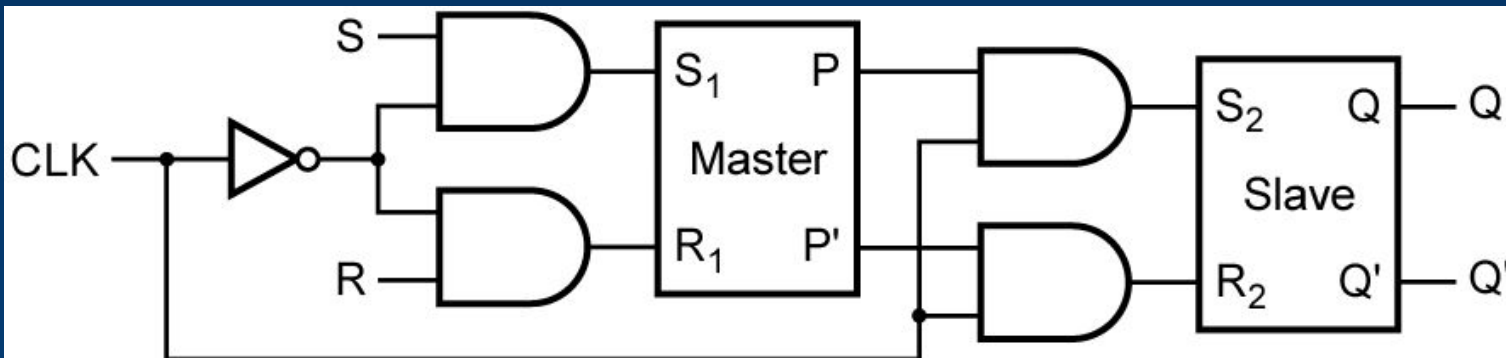


(a) Implementation with two latches

 

(b) Timing analysis

# J-K Flip-Flop(1/2)

 


(a) J-K flip-flop


$$Q^+ = JQ' + K'Q$$

<i>J</i>	<i>K</i>	<i>Q</i>	<i>Q</i> <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

# J-K Flip-Flop(2/2)

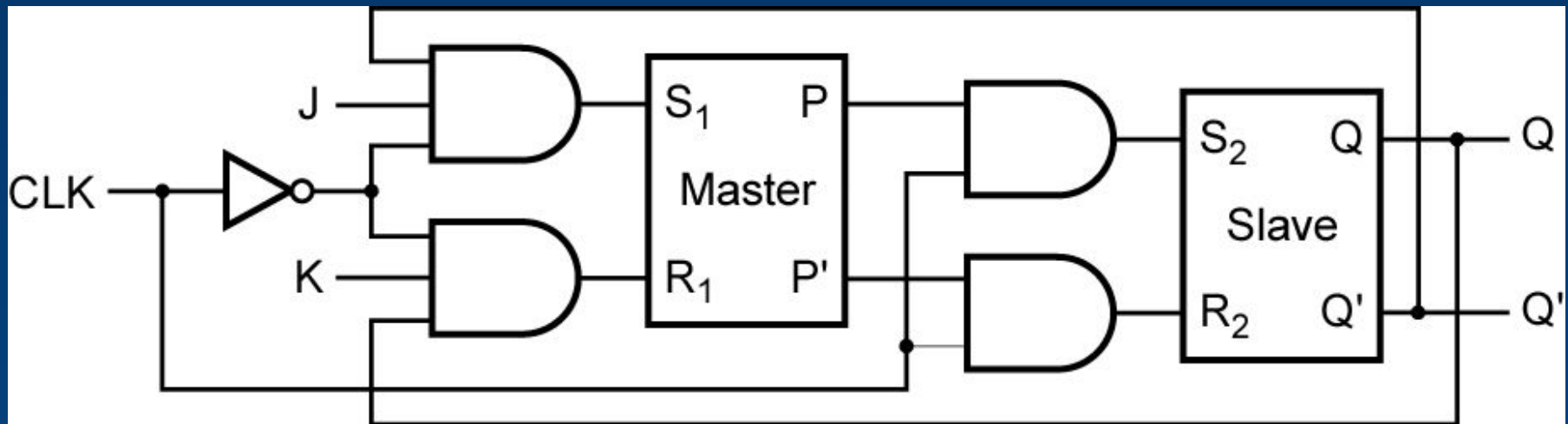


# T Flip-Flop(1/2)

 


$T$	$Q$	$Q^+$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^+ = T'Q + TQ' = Q \oplus T$$

# T Flip-Flop(2/2)

 

(a) Conversion of J-K to T

 

(b) Conversion of D to T

# Boolean Algebra for Flip-Flops

$$\text{D flip-flop } Q^+ = D \quad (13-1)$$


$$\text{D-CE flip-flop } Q^+ = D \cdot CE + Q \cdot CE' \quad (13-2)$$

$$\text{T flip-flop } Q^+ = T \oplus Q \quad (13-3)$$

$$\text{S-R flip-flop } Q^+ = S + R'Q \quad (13-4)$$


$$\text{J-K flip-flop } Q^+ = JQ' + K'Q \quad (13-5)$$

# Digital內建的正反器

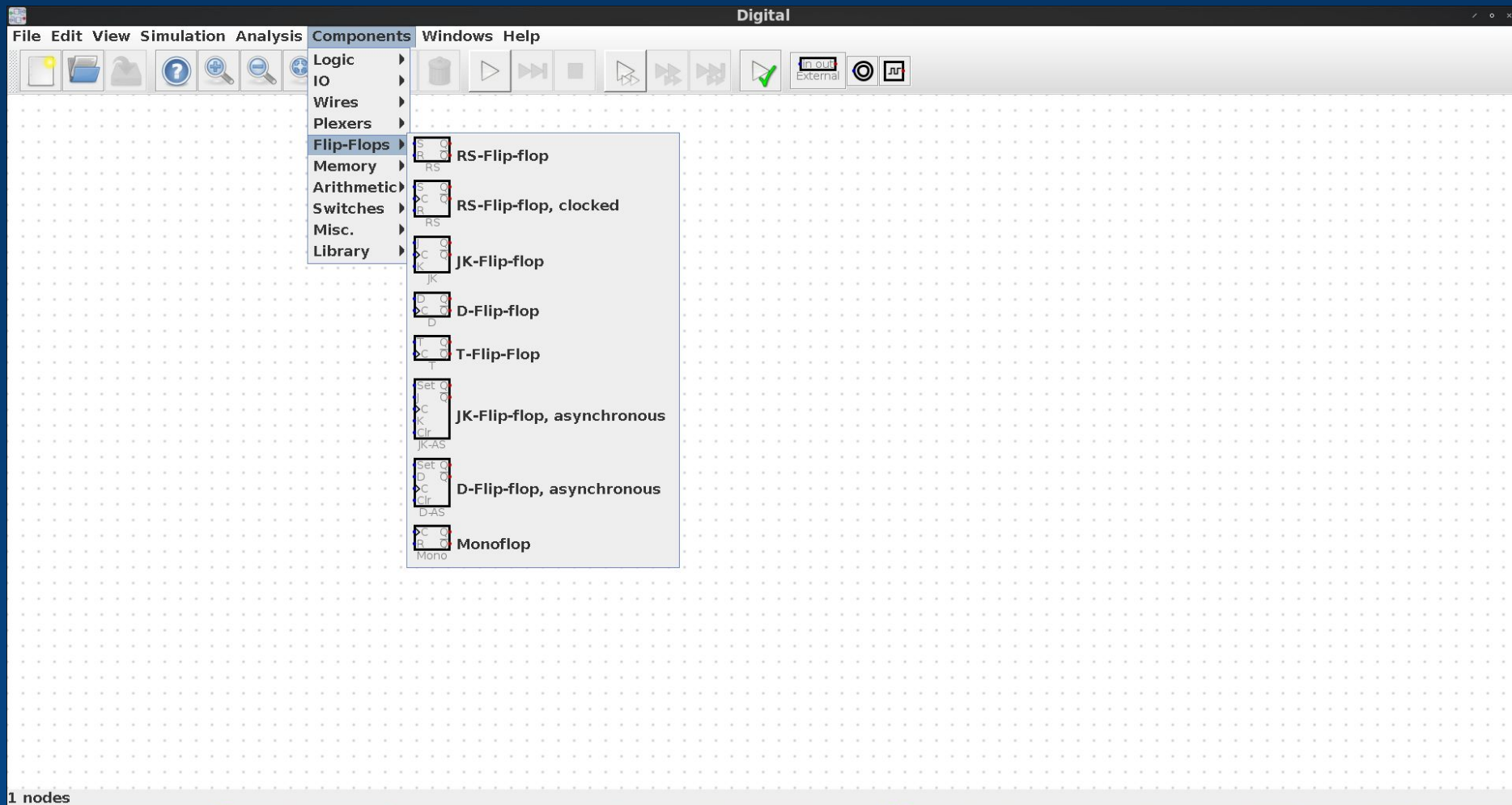



# Digital內的時脈產生器

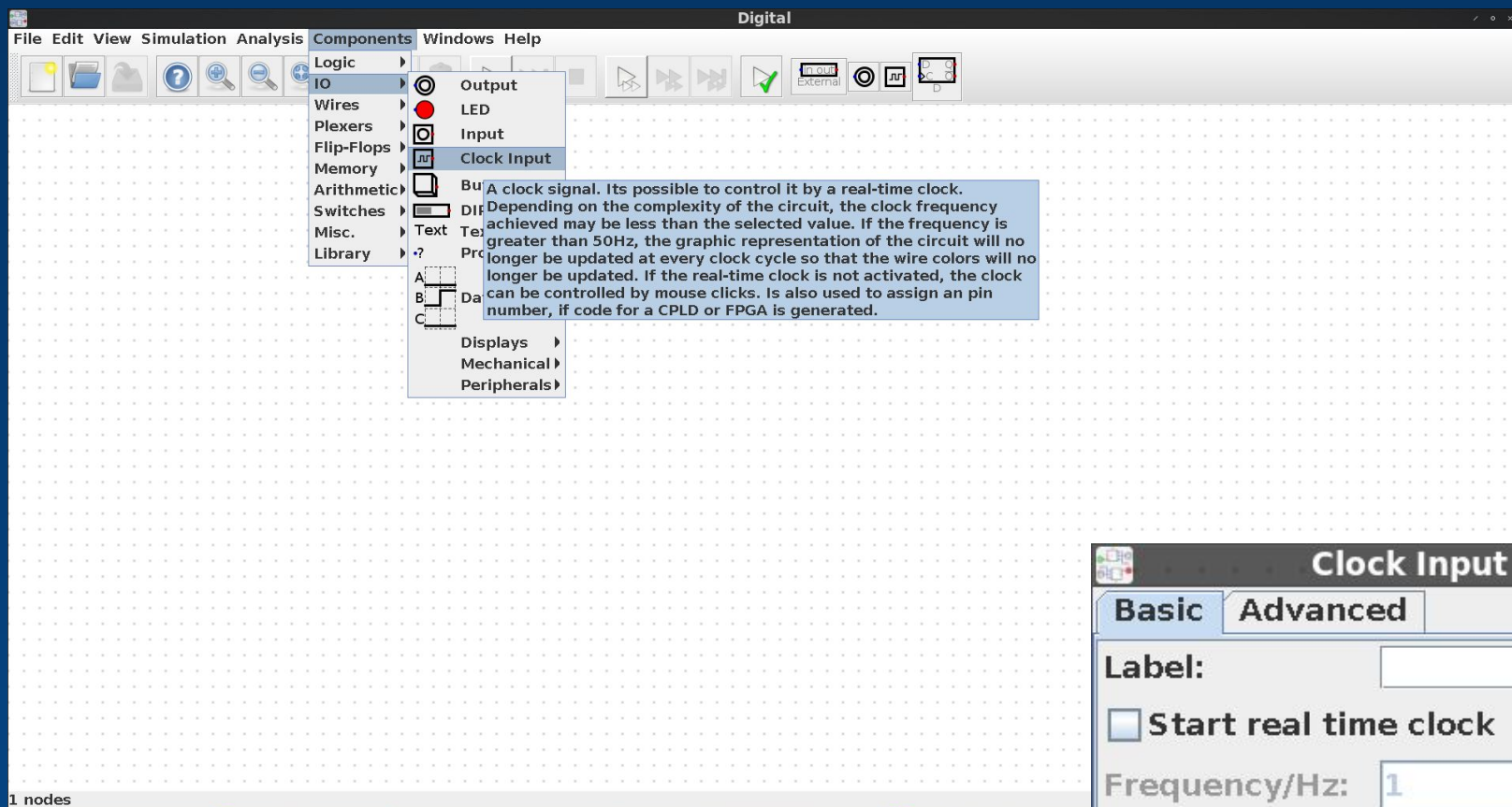


# Modeling Flip-Flops Using Processes

A flip-flop can change state either on the rising or on the falling edge of the clock input. This type of behavior is modeled in VHDL by a process.

Section 17.1 (p. 554)

## Modeling Flip-Flops Using Processes

 

```
process (CLK)
begin
    if CLK'event and CLK = '1' -- rising edge of CLK
        then Q <= D;
    end if;
end process;
```

Figure 17-1: VHDL Code for a Simple D Flip-Flop

# Modeling Flip-Flops Using Processes

A basic process has the following form:


```
process(sensitivity-list)
begin
    sequential-statements
end process;
```

The basic **if** statement has the form:

```
if condition then
    sequential statements1
else sequential statements2
end if;
```

**Section 17.1 (p. 554)**

## Modeling Flip-Flops Using Processes

 


```

process (G,D)
begin
    if G = '1' then Q <= D; end if;
end process;
  
```

Figure 17-2: VHDL Code for a Transparent Latch

## Modeling Flip-Flops Using Processes

 

```
process (CLK, ClnN)
begin
    if ClnN = '0' then Q <= '0';
        else if CLK'event and CLK = '1'
            then Q <= D;
            end if;
        end if;
end process;
```

Figure 17-3: VHDL Code for a D Flip-Flop with Asynchronous Clear

# Modeling Flip-Flops Using Processes

The most general form of the **if** statement is

```
if condition then
    sequential statements
{elsif condition then
    sequential statements}
-- 0 or more elsif clauses may be included
[else sequential statements]
end if;
```

The curly brackets indicate that any number of **elsif** clauses may be included, and the square brackets indicate that the **else** clause is optional.

**Section 17.1 (p. 554)**

## Modeling Flip-Flops Using Processes


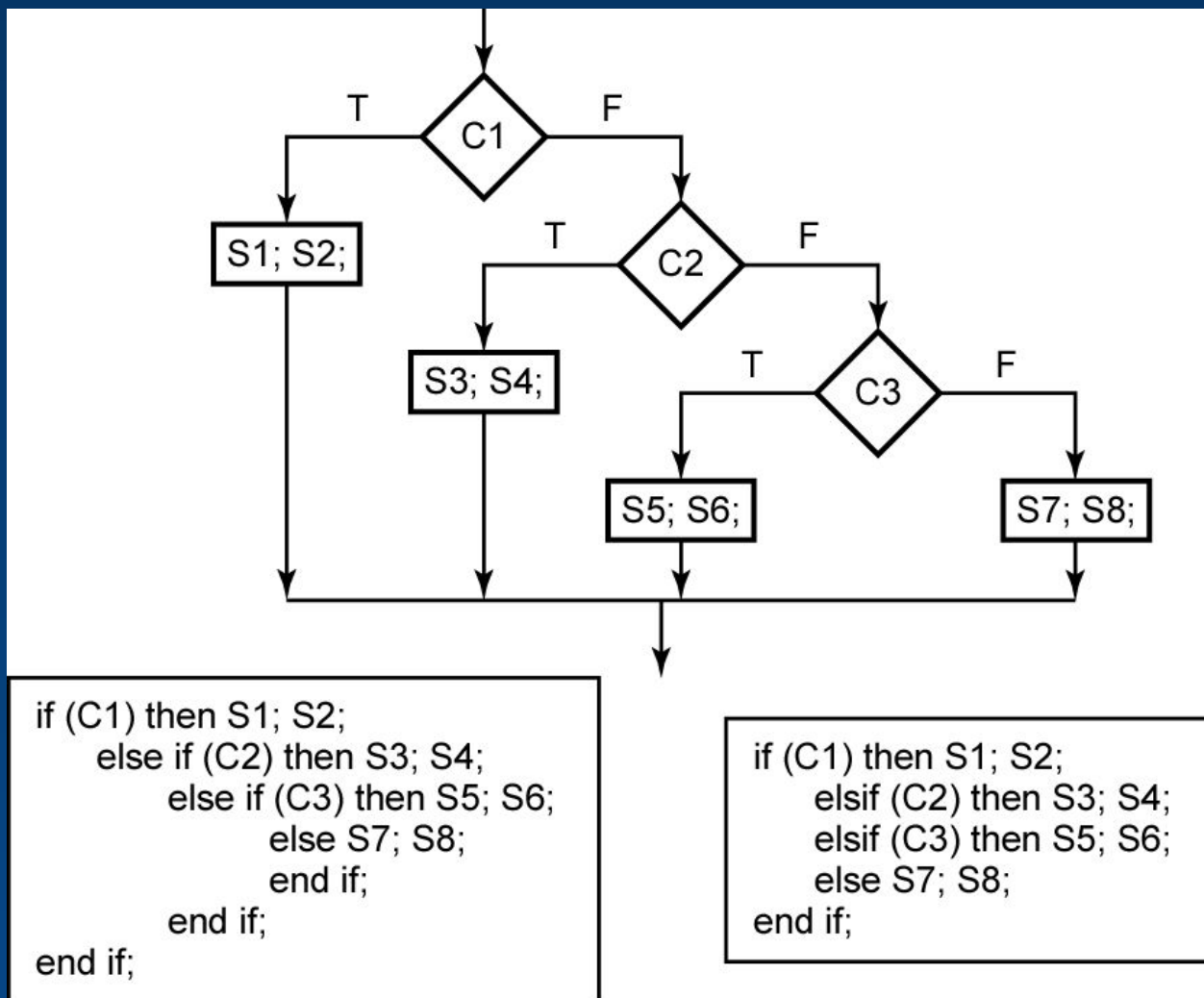


Figure 17-4: Equivalent Representations of a Flow Chart Using Nested Ifs and Elsifs

 

## Modeling Flip-Flops Using Processes



$$Q^+ = JQ' + K'Q$$

Figure 17-5: J-K Flip-Flop

# Modeling Flip-Flops Using Processes

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
USE ieee.numeric_std.all;
```

```
entity JKFF is
```

```
port (SN, RN, J, K, CLK: in std_logic;
```

```
      Q, QN: out std_logic);
```

```
end JKFF;
```

## Modeling Flip-Flops Using Processes

**architecture JKFF1 of JKFF is**

**signal** Qint: std\_logic; -- internal value of Q

**begin**

Q <= Qint; -- output Q and QN to port

QN <= not Qint;

**process** (SN, RN, CLK)

**begin**

**if** RN = '0' **then** Qint <= '0'; -- RN='0' will clear the FF

**elsif** SN = '0' **then** Qint <= '1'; -- SN='0' will set the FF

**elsif** CLK'event **and** CLK = '0' **then** -- falling edge of CLK


Qint <= (J **and** not Qint) **or** (not K **and** Qint);

**end if;**

**end process;**

**end JKFF1;**

## Modeling Flip-Flops Using Processes

 


```

process (CLK)
begin
    if CLK'event and CLK = '1' then
        Q1 <= Q3 after 5 ns;
        Q2 <= Q1 after 5 ns;
        Q3 <= Q2 after 5 ns;
    end if;
end process;
    
```

Figure 17-7: Cyclic Shift Register

## Modeling Flip-Flops Using Processes

 


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;
```

```
entity my_DFF is
port (D, clk: in std_logic;
      Q: out std_logic);
end my_DFF;
```

```
architecture DFF_simple of my_DFF is
begin
    process (clk)
    begin
        if clk'event and clk = '1' then
            Q <= D after 5 ns;
        end if;
    end process;
end DFF_simple;
```

Figure 17-8a: Structural VHDL Code for Cyclic Shift Register

## Modeling Flip-Flops Using Processes

 

```


LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;
  
```

```

entity cyclicSR is
port (clk: in std_logic;
      Qout: out std_logic_vector(1 to 3));
end cyclicSR;
  
```

Figure 17-8b: Structural VHDL Code for Cyclic Shift Register

## Modeling Flip-Flops Using Processes

 

architecture cyclicSR3 of cyclicSR is  
component my\_DFF

port (D, clk: in std\_logic;

Q: out std\_logic);

end component;

signal Q1, Q2, Q3: std\_logic;

begin

FF1: my\_DFF port map (Q3, clk, Q1);

FF2: my\_DFF port map (Q1, clk, Q2);

FF3: my\_DFF port map (Q2, clk, Q3);

Qout <= Q1 & Q2 & Q3;

end cyclicSR3;

Figure 17-8b: Structural VHDL Code for Cyclic Shift Register


# 作業題(1/2)

- 作業題1:請利用以下兩種方式實作S-R正反器
- 方法一:利用NOR邏輯閘實作投影片第3頁的S-R Latch, 將完成的S-R Latch模組化之後, 實作投影片第10與12頁的S-R正反器。
- 方法二:利用VHDL Process實作S-R正反器
- 比較投影片第10頁的波型圖與兩個方法實作S-R正反器的波形圖。
- 請挑戰修正投影片第10頁中紅色區域的錯誤。


 
# 作業題(2/2)

- 作業題2: 請利用以下兩種方式實作 $A$ - $B$ 正反器
- 方法一利用VHDL Process實作 $A$ - $B$ 正反器
- 方法二利用作業題1的 $S$ - $R$ 正反器實作 $A$ - $B$ 正反器



$A$	$B$	$Q^+$
0	0	0
0	1	$Q$
1	0	$Q'$
1	1	1